


# Arithmetic

# Addition and Subtraction of Signed Numbers

$x_i$	$y_i$	Carry-in $c_i$	Sum $s_i$	Carry-out $c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \overline{x_i} \overline{y_i} c_i + \overline{x_i} y_i \overline{c_i} + x_i \overline{y_i} \overline{c_i} + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$
$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

 Example:

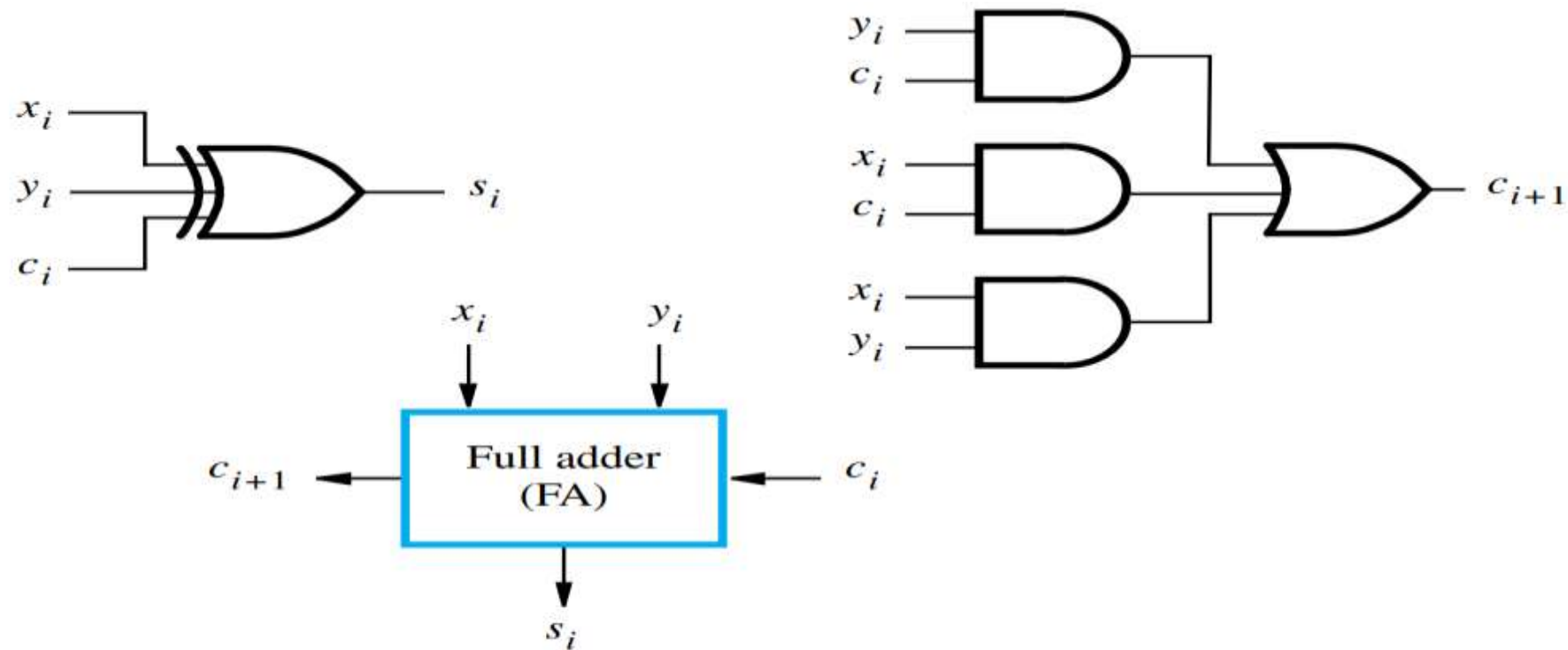


**Figure 9.1** Logic specification for a stage of binary addition.

Figure shows the truth table for the sum and carry-out functions for adding equally weighted bits  $x_i$  and  $y_i$  in two numbers X and Y .


The logic expression for  $s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$

in can be implemented with a 3-input XOR gate, used in Figure 9.2a as part of the logic required for a single stage of binary addition. The carry-out function,  $c_{i+1}$ , is implemented with an AND-OR circuit, as shown. A convenient symbol for the complete circuit for a single stage of addition, called a full adder (FA), is also shown in the figure.



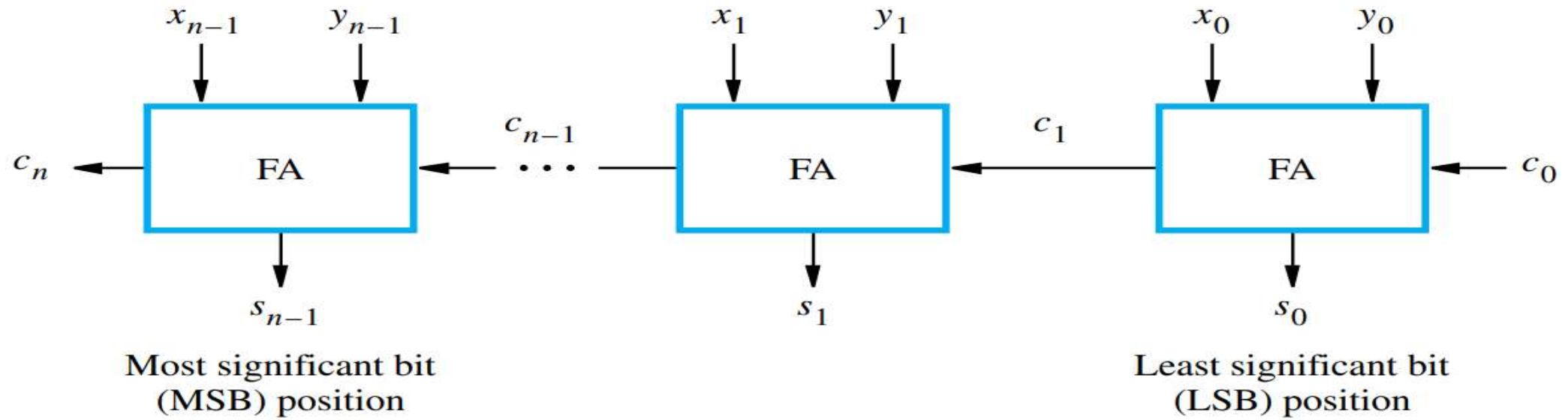(a) Logic for a single stage


A cascaded connection of  $n$  full-adder blocks can be used to add two  $n$ -bit numbers, as shown in Figure 9.2b. Since the carries must propagate, or ripple, through this cascade, the configuration is called a ripple-carry adder.



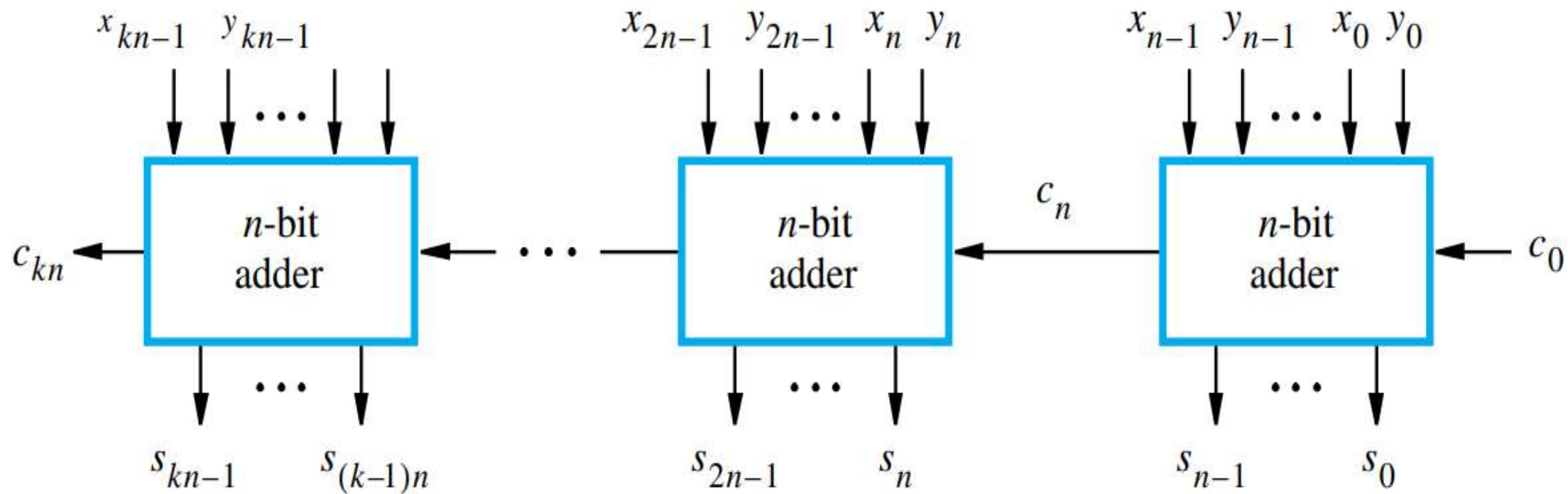(b) An  $n$ -bit ripple-carry adder

The carry-in,  $c_0$ , into the least-significant-bit (LSB) position provides a convenient means of adding 1 to a number. For instance, forming the 2's-complement of a number involves adding 1 to the 1's-complement of the number.

The carry signals are also useful for interconnecting  $k$  adders to form an adder capable of handling input numbers that are  $kn$  bits long,



(c) Cascade of  $k$   $n$ -bit adders

## Addition/Subtraction Logic Unit

The n-bit adder can be used to add 2's-complement numbers X and Y , where the  $x_{n-1}$  and  $y_{n-1}$  bits are the sign bits.

The carry-out bit  $c_n$  is not part of the answer. Because Arithmetic overflow occurs when the signs of the two operands are the same, but the sign of the result is different. Therefore, a circuit to detect overflow can be added to the n-bit adder by implementing the logic expression

$$\text{Overflow} = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$

It can also be shown that overflow occurs when the carry bits  $c_n$  and  $c_{n-1}$  are different.


Therefore, a simpler circuit for detecting overflow can be obtained by implementing the expression  $c_n \oplus c_{n-1}$  with an XOR gate.

In order to perform the subtraction operation  $X - Y$  on 2's-complement numbers X and Y , we form the 2's-complement of Y and add it to X .

The logic circuit can be used to perform either addition or subtraction based on the value applied to the Add/Sub input control line.

This line is set to 0 for addition, applying Y unchanged to one of the adder inputs along with a carry-in signal,  $c_0$ , of 0.

When the Add/Sub control line is set to 1, the Y number is 1's-complemented (that is, bit-complemented) by the XOR gates and  $c_0$  is set to 1 to complete the 2's-complementation of Y. An XOR gate can be added detect the overflow condition  $c_n \oplus c_{n-1}$

 

**Figure 9.3** Binary addition/subtraction logic circuit.

## Design of Fast Adders

A carry-look ahead adder (CLA) or fast adder is a type of adder used in digital logic.

A carry-look ahead adder improves speed by reducing the amount of time required to determine carry bits.

- If n-bit ripple carry adder is used in Add/ Sub Circuit, it may have too much delay in producing output.
- This delay is mainly because of carry.
- So we need to find a better parallel method to calculate carry.

Ex: rather than waiting for c3 directly generate C4 , so we need to design a circuit.

A fast adder circuit must speed up the generation of the carry signals. The logic expressions for  $s_i$  (sum) and  $c_{i+1}$  (carry-out) of stage  $i$  are

$$\begin{aligned} s_i &= x_i \oplus y_i \oplus c_i \\ c_{i+1} &= x_i y_i + x_i c_i + y_i c_i \end{aligned}$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$\begin{aligned} c_{i+1} &= G_i + P_i c_i \\ \text{where } G_i &= x_i y_i \text{ and } P_i = x_i + y_i \end{aligned}$$



$G_i$  is called generate function and  $P_i$  is called propagate function for stage


generate function for stage  $i$  is equal to 1, then  $c_{i+1} = 1$ , independent of the input carry,  $c_i$ . This occurs when both  $x_i$  and  $y_i$  are 1.


- $G_i$  and  $P_i$  are computed only from  $x_i$  and  $y_i$  and not  $c_i$ , thus they can be computed in one gate delay after  $X$  and  $Y$  are applied to the inputs of an  $n$ -bit adder.
- Expanding  $c_i$  in terms of  $i - 1$  subscripted variables and substituting into the  $c_{i+1}$  expression, we obtain  $c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} c_{i-1}$

Continuing this type of expansion, the final expression for any carry variable is

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

 - All sums can be obtained 1 gate delay after the carries are computed.
- Independent of  $n$ ,  $n$ -bit addition requires only 4 gate delays.
- This is called Carry Lookahead adder.



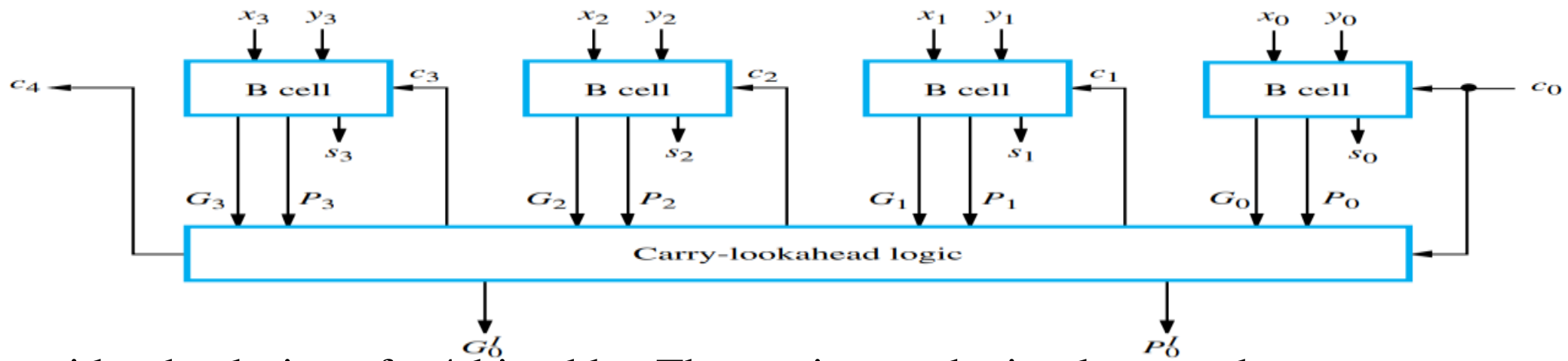

Let us consider the design of a 4-bit adder. The carries can be implemented as

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

- These equations suggest that  $C_1, C_2, C_3$  &  $C_4$  can be generated directly from  $C_0$ .  
i.e. these 4 carries depends on initial carry  $C_0$ .

For this reason these equations are called carry-look ahead equations.

Performing  $n$ -bit addition in 4 gate delays independent of  $n$  is good.

CLA is a high speed adder , which adds 2 numbers without waiting for the carries from the previous stages.

In CLA, carry inputs of all stages are generated simultaneously, without using carries from the previous stages.

### Higher-Level Generate and Propagate Functions

a 16-bit adder built from four 4-bit adder blocks.

These blocks provide new output functions defined as  $G_k^I$  and  $P_k^I$  , where  $k = 0$  for the first 4-bit block,  $k = 1$  for the second 4-bit block, and so on,


In the first block,  $P_0^I = P_3P_2P_1P_0$

and  $G_0^I = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$

*Subscript I denotes the blocked carry look ahead and identifies the block*

Carry  $c_{16}$  is formed by one of the carry-look ahead circuits in fig
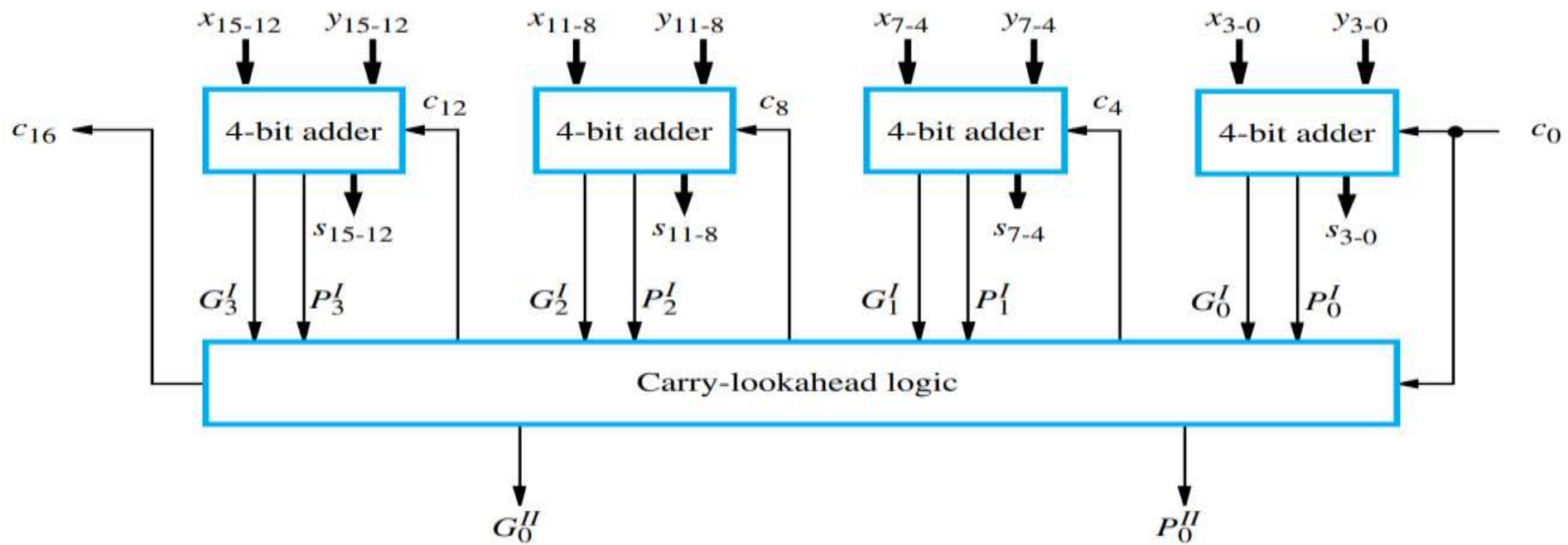
$$c_{16} = G_3^I + P_3^I G_2^I + P_3^I P_2^I G_1^I + P_3^I P_2^I P_1^I G_0^I + P_3^I P_2^I P_1^I P_0^I c_0$$



After  $x_i, y_i$  and  $c_0$  are applied as inputs:

- -  $G_i$  and  $P_i$  for each stage are available after 1 gate delay.
- -  $P^I$  is available after 2 and  $G^I$  after 3 gate delays.
- - All carries are available after 5 gate delays.
- -  $c_{16}$  is available after 5 gate delays.
- -  $s_{15}$  which depends on  $c_{12}$  is available after 8 (5+3)gate delays
- (Recall that for a 4-bit carry lookahead adder, the last sum bit is available 3 gate delays after all inputs are available)

## Multiplication of Unsigned Numbers

- Multiplication of two unsigned binary numbers of  $n$  bit size results into  $2n$  bit result.
- In binary system, multiplication of the multiplicand by multiplier, if multiplier is 1 then multiplicand is entered in appropriate shifted position and if the multiplier is 0 then 0s are entered in appropriate shifted position.
- Let us consider a Multiplicand of 4 bit size as  $(A_3, A_2, A_1, A_0)$  and Multiplier of 4 bit size as  $(B_3, B_2, B_1, B_0)$ . Multiplication of these two is as shown below

A3	A2	A1	A0		- Multiplicand
X	B3	B2	B1	B0	- Multiplier

3B0 A2B0 A1B0 A0B0      Partial Products (PP)

$$+ A_3B_1 A_2B_1 A_1B_1 A_0B_1$$
$$+ A_3B_2 A_2B_2 A_1B_2 A_0B_2$$
$$+ A_3B_3 \ A_2B_3 \ A_1B_3 \ A_0B_3$$

P7   P6   P5   P4   P3   P2   P1   P0                      - Products

Where (P7,P6.....P0) are product terms generated by adding the partial products as below

- $P_0 = A_0B_0$
- $P_1 = A_1B_0 + A_0B_1 + \text{Carryout of } P_0$
- $P_2 = A_2B_0 + A_1B_1 + A_0B_2 + \text{Carryout of } P_1$
- $P_3 = A_3B_0 + A_2B_1 + A_1B_2 + A_0B_3 + \text{Carryout of } P_2$
- $P_4 = A_3B_1 + A_2B_2 + A_1B_3 + \text{Carryout of } P_3$
- $P_5 = A_3B_2 + A_2B_3 + \text{Carryout of } P_4$
- $P_6 = A_3B_3 + \text{Carryout of } P_5$
- $P_7 = \text{Carryout of } P_6$


$$\begin{array}{r}
 \phantom{0000}1\phantom{00}1\phantom{00}0\phantom{00}1 \\
 \phantom{000}\times\phantom{00}1\phantom{00}0\phantom{00}1\phantom{00}1 \\
 \hline
 \phantom{0000}1\phantom{00}1\phantom{00}0\phantom{00}1 \\
 \phantom{000}1\phantom{00}1\phantom{00}0\phantom{00}1 \\
 \phantom{00}0\phantom{00}0\phantom{00}0\phantom{00}0 \\
 \phantom{0}1\phantom{00}1\phantom{00}0\phantom{00}1 \\
 \hline
 1\phantom{00}0\phantom{00}0\phantom{00}0\phantom{00}1\phantom{00}1\phantom{00}1\phantom{00}1
 \end{array}
 \begin{array}{l}
 (13) \text{ Multiplicand M} \\
 (11) \text{ Multiplier Q} \\
 \\
 \\
 \\
 (143) \text{ Product P}
 \end{array}$$

(a) Manual multiplication algorithm
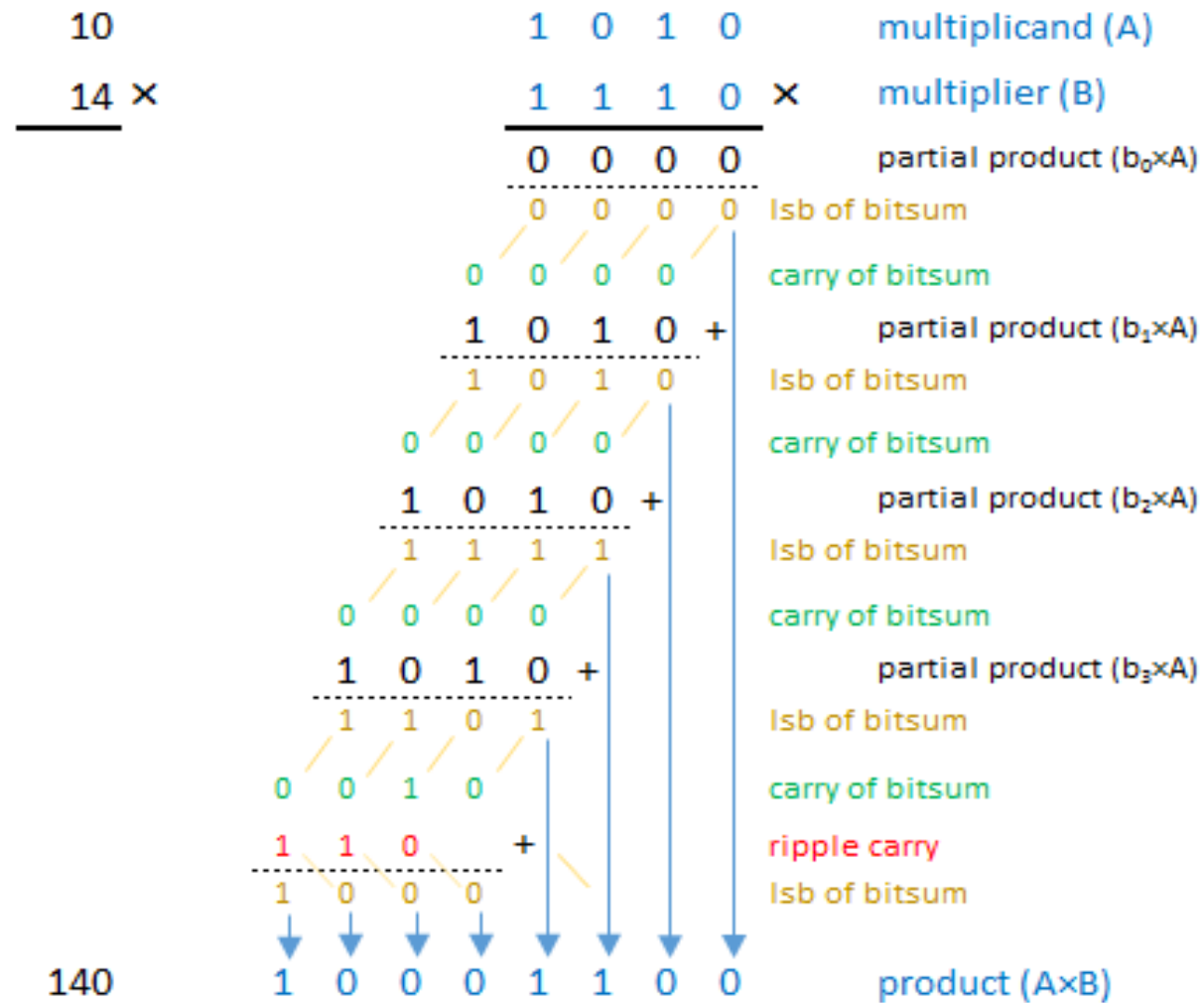
## Array multiplier

- Array multiplier is well known due to its regular structure. Multiplier circuit is based on add and shift algorithm.
- Each partial product is generated by the multiplication of the multiplicand with one multiplier bit. The partial product are shifted according to their bit orders and then added.

The addition can be performed with normal carry propagate adder. N-1 adders are required where N is the multiplier length.




				A3	A2	A1	A0	Inputs
x				B3	B2	B1	B0	
C				B0 x A3	B0 x A2	B0 x A1	B0 x A0	Internal Signals
+		B1 x A3	B1 x A2	B1 x A1	B1 x A0			
C				sum	sum	sum	sum	
+		B2 x A3	B2 x A2	B2 x A1	B2 x A0			
C				sum	sum	sum	sum	
+		B3 x A3	B3 x A2	B3 x A1	B3 x A0			
C				sum	sum	sum	sum	Outputs
Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0	



Binary Multiplication product terms can be implemented by using cells consisting of

 
- a) AND gate – Used for producing Partial Products (PP)  $q_i.m_j$  &
- b) Full Adder (FA) – Used to produce product terms by summation of PPs





$$A = a_3a_2a_1a_0$$

$$B = b_3b_2b_1b_0$$

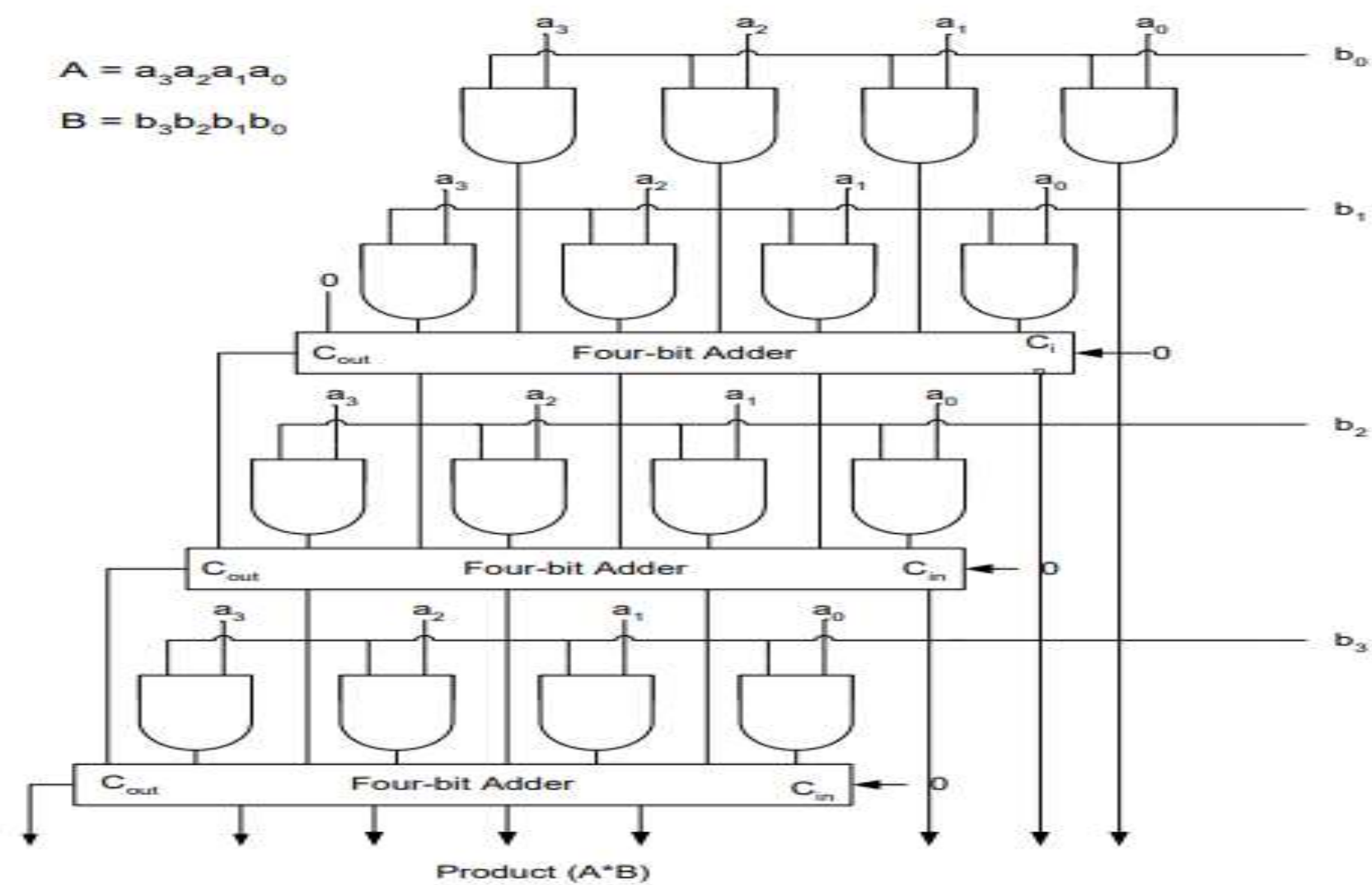

## Advantages:

- Array Multiplier is a Parallel Multiplier where the worst time propagation delay is through critical
- path with  $6(n-1)-1$  gate delay including the initial AND gate delay in all cells, for an  $n \times n$  array.


## Drawback:

- Hardware resource used is high i.e., it uses a large number of logic gates for multiplying numbers of practical size, such as 32- or 64-bit numbers
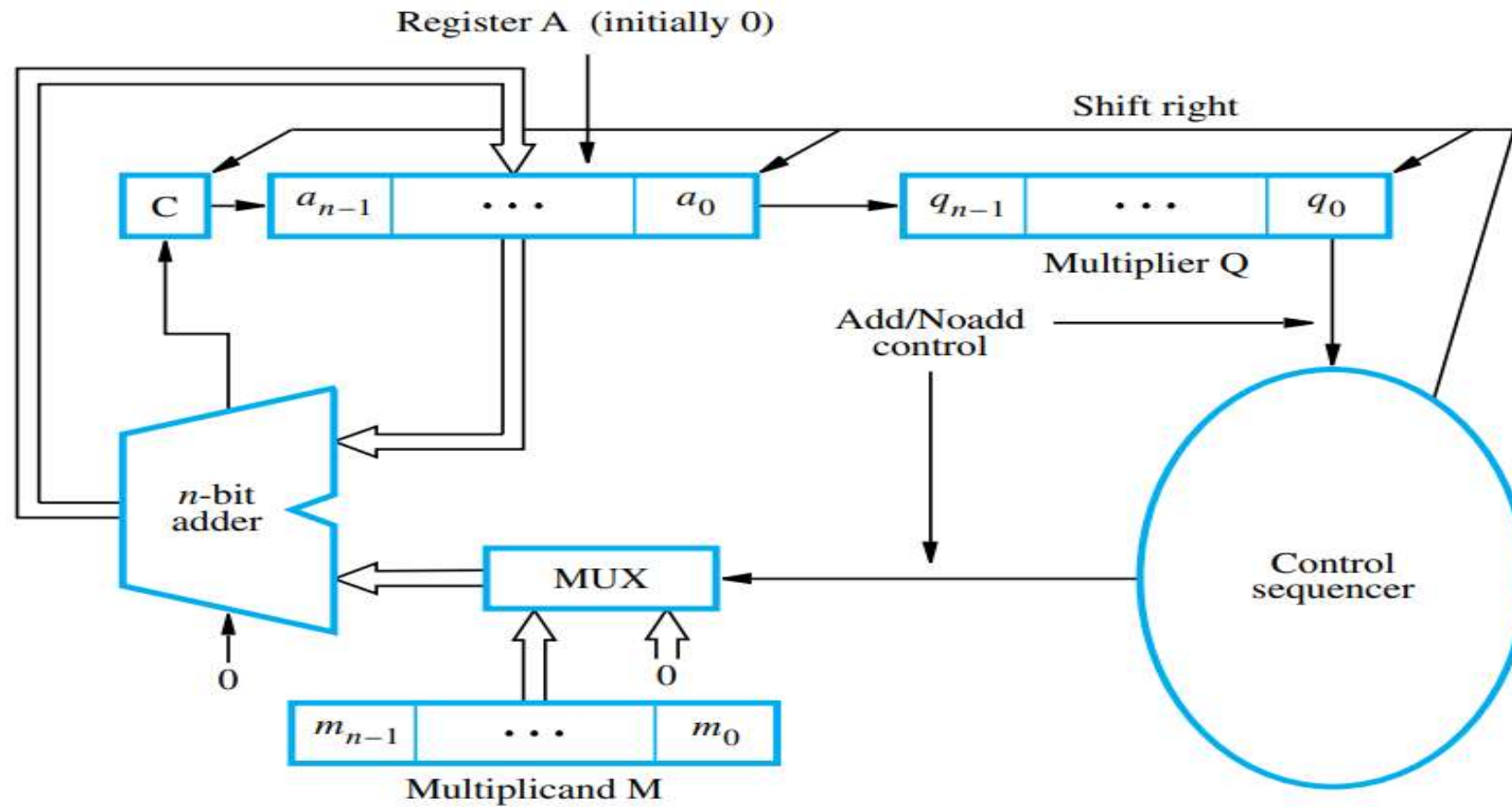
## Sequential Circuit Multiplier

- This circuit performs multiplication by using
- Single  $n$ -bit adder  $n$  times to implement the spatial addition performed by the  $n$  rows of ripple-carry adders in array multiplier.
- Registers A and Q are shift registers, concatenated as shown, they hold partial product  $PP_i$  while multiplier bit  $q_i$  generates the signal Add/No add.

- This signal causes the multiplexer MUX to select 0 when  $q_i = 0$ , or to select the multiplicand  $M$  when  $q_i = 1$ , to be added to  $PP_i$  to generate  $PP(i + 1)$ . The product is computed in  $n$  cycles. Initially Register A is loaded with  $PP_i$  as 0s ( $n$  bit 0s)
- The Sequential Circuit Multiplier is as shown in Figure




(a) Register configuration
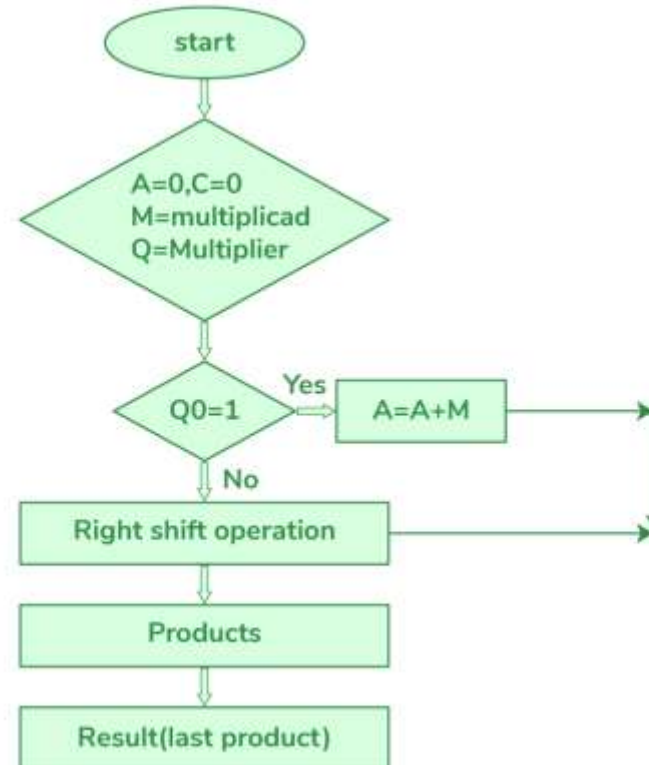
## Sequential Circuit Multiplier

The flow chart explains the whole operation of the sequential binary multiplier in a simple manner. First, assign 0 to the accumulator(A) and carry(C) values. then check the LSB of Q(multiplier) i.e  $Q_0$ , if  $q_0$  is 0 then perform only the right shift operation and if  $q_0$  is 1 then perform the addition of the accumulator and multiplicand, store the result in the accumulator then perform the right shift operation.


We have to continue this process based on the number of bits in the multiplier.



- Example: Let us consider two 4 bit number multiplication  $(1101)_2 \times (1011)_2$

$$\begin{array}{r}
 \phantom{000}1101 \\
 \times 1011 \\
 \hline
 \phantom{000}1101 \\
 \phantom{00}0000 \\
 \phantom{0}0000 \\
 1101 \\
 \hline
 10001111
 \end{array}$$

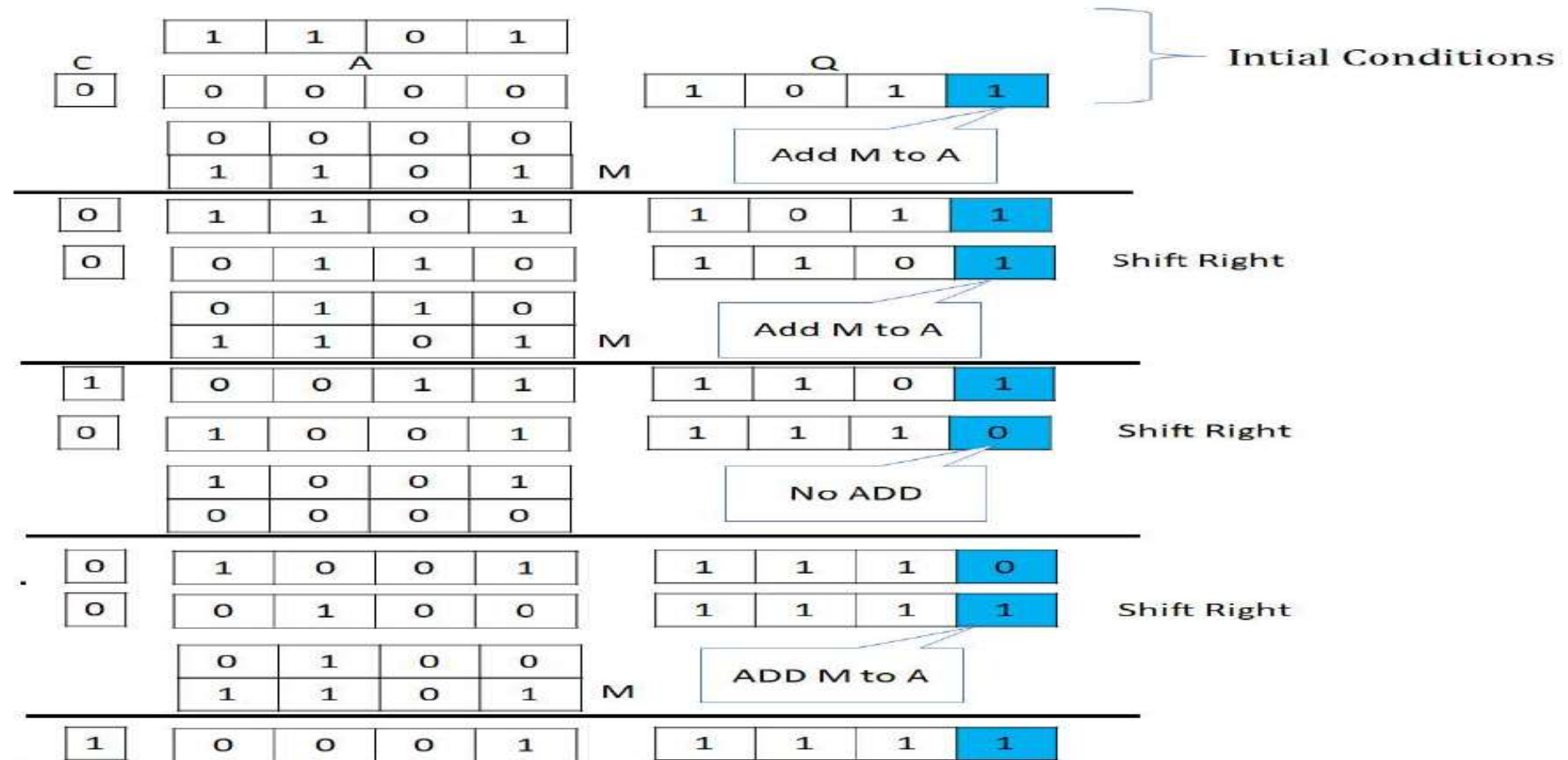(13) Multiplicand M  
(11) Multiplier Q  
(143) Product P



## Multiplication of Signed Numbers

- Case (1): Consider a positive multiplier and a negative multiplicand.

When Multiplier bit is 1, the Multiplicand is added to Partial Product (PP<sub>i</sub>). In this case, we must extend the sign-bit value of the multiplicand to the left as far as the product will extend.

- Example: Let us consider a 5-bit signed operands: – A multiplicand: (-13) and a multiplier: (+11) produces 10-bit product, (-143). The Multiplication is

						1	0	0	1	1	-13
					×	0	1	0	1	1	+11
Sign Extended	1	1	1	1	1	1	0	0	1	1	
Sign Extended	1	1	1	1	1	0	0	1	1		
						0	0	0	0	0	
Sign Extended	1	1	1	0	0	1	1				
						0	0	0	0	0	
Result	1	1	0	1	1	1	0	0	0	1	

Case II : Both are non negative numbers (+ve) ,then same multiplication as using unsigned numbers

- Case III : Consider a Negative Multiplier and a Negative Multiplicand

In this case, need to take 2's-complements of both the multiplier and the multiplicand and proceed as in the case of a positive multiplier.

This is possible because complementation of both operands does not change the value or the sign of the product.

Case IV : both negative and negative take 2's complement of both( $-3 * -7 = +3 * +7$ )

## Booths multiplication algorithm

- The Booth Algorithm treats both positive and negative 2's complement n-bit operands uniformly.
- Basic principle used in Booth Algorithm is to reduce the number of operations is as follows  
A multiplier may be positive / negative.
- In Booth Algorithm, the multiplier is modified such that the number of operation is reduced as follows.

### Booth Recoding of Multiplier


Multiplier		Version of multiplicand selected by bit $i$
Bit $i$	Bit $i - 1$	
0	0	$0 \times M$
0	1	$+ 1 \times M$
1	0	$- 1 \times M$
1	1	$0 \times M$




In general, in the Booth algorithm, the recoding of the Multiplier is done as follows

- $-1$  times the shifted multiplicand is selected when moving from 0 to 1, and
- $+1$  times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

Example 1: Recoding of Multiplier (0 0 1 1 1 1 0)<sub>2</sub>

 

 Example 2: Recoding of Multiplier (0 0 1 0 1 1 0 0 1 1 1 0 1 0 1 1 0 0)<sub>2</sub>




Let us take a Multiplicand – (0101101) and Multiplier (0011110)


									0	1	0	1	1	0	1
									0	0 + 1	+ 1	+ 1	+ 1	+ 1	0
									0	0	0	0	0	0	0
						0			1	0	1	1	0	1	
					0	1			0	1	1	0	1		
				0	1	0			1	1	0	1			
			0	1	0	1			1	0	1				
		0	0	0	0	0			0	0					
	0	0	0	0	0	0			0						
0	0	0	1	0	1	0	1	0	0	0	0	1	1	0	

								0	1	0	1	1	0	1
							X	0	+1	0	0	0	-1	0
2's compl	0	0	0	0	0	0	0	0	0	0	0	0	0	0
	1	1	1	1	1	1	0	1	0	0	1	1		
	0	0	0	0	0	0	0	0	0	0	0	0		
	0	0	0	0	0	0	0	0	0	0	0			
	0	0	0	0	0	0	0	0	0	0				
	0	0	0	0	0	0	0	0	0					
	0	0	0	1	0	1	1	0	1					
	0	0	0	0	0	0	0							
	0	0	0	1	0	1	0	1	0	0	0	1	1	0

This leads to reduced operations

 

 - Best case – a long string of 1's (skipping over 1s)
- Worst case – 0's and 1's are alternating



## Fast Multiplication

- There are two techniques discussed for speeding the Multiplication Operation
  - i. Reducing Maximum number of Summands: - Bit Pair Recoding of Multipliers reduces the maximum number of summands ( versions of multiplicand ) that must be added to  $n/2$  for  $n$  bit operands.
  - ii. Faster Summands addition: - Summand addition uses
    - a) Carry save – In this carry generated by Full Adders in  $i$ th row propagated to  $(i+1)$ th row Full Adders instead of rippling through adder in same row and
    - b) Summands Reduction Technique - Techniques like 3 to 2, 4 to 2 reduction of summands .


Reducing Maximum number of Summands using Bit Pair Recoding of Multipliers

- Bit-pair recoding of the multiplier – It is a modified Booth Algorithm, In this it uses one summand for each pair of booth recoded bits of the multiplier. (reduce the multiplier bits if  $n$  bits are there in multiplier we get  $n$  summands ,  $n$  summands are reduced to  $n/2$ )

Step 1: Convert the given Multiplier into a Booth Recode the Multiplier . In booths recoding we get 2 bits i.e..bit  $i$  & bit  $i-1$ , but in bit pair reducing we get 3 bits i.e..  $i-1, i, i+1$

Step 2: Group the recoded Multiplier bits in pairs and observe the following

Multiplier bit-pair		Multiplier bit on the right	Multiplicand selected at position $i$
$i + 1$	$i$		
0	0	0	$0 \times M$
0	0	1	$+1 \times M$
0	1	0	$+1 \times M$
0	1	1	$+2 \times M$
1	0	0	$-2 \times M$
1	0	1	$-1 \times M$
1	1	0	$-1 \times M$
1	1	1	$0 \times M$

 

(a) Example of bit-pair recoding derived from Booth recoding

Here  $-1 * M$  means 2's complement of  $M$

$+2*M$  means first place 0 in LSB and multiply  $M$  with 1


$-2*M$  means first place 0 in LSB and 2's complement of  $M$

- Now let us see how bit pair Recoding Multiplier (Modified Booth) reduces the number of summands in comparison with Booth Recoding Multiplier algorithm

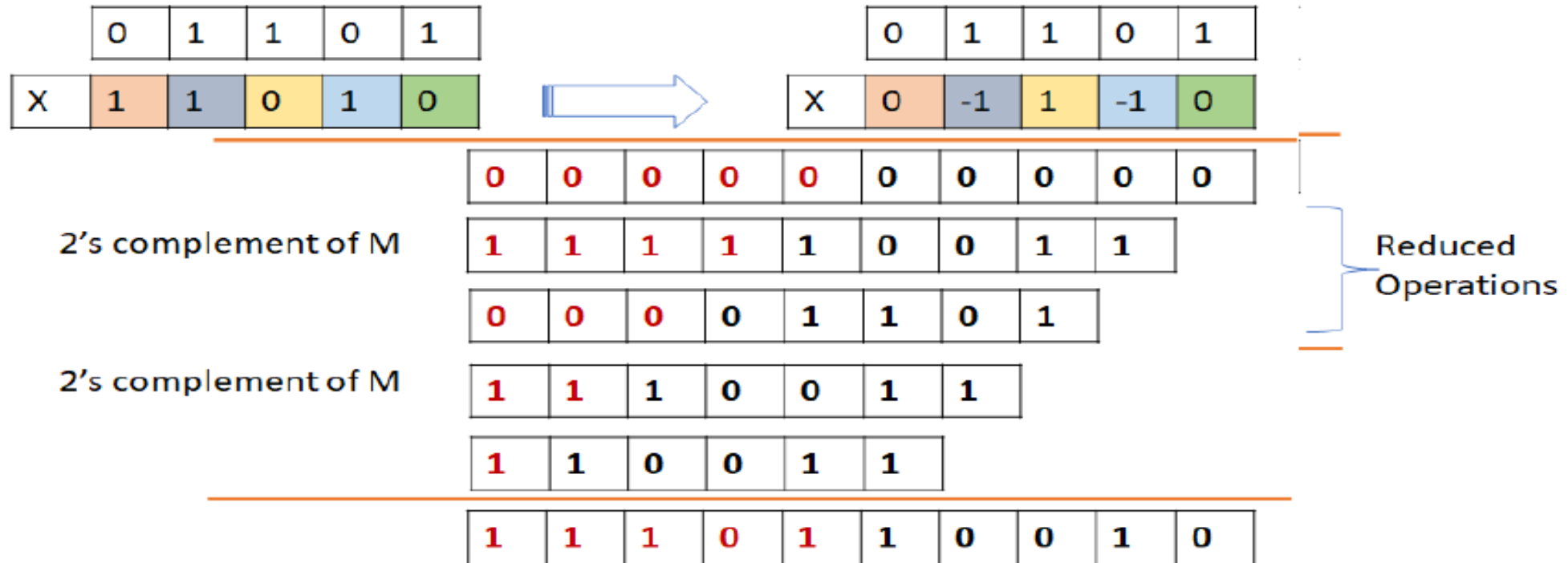Example : Multiplication of  $(+13) = (01101)_2$  by  $(-6) = (11010)_2$

By Booth Recoding of Multiplier  $(1\ 1\ 0\ 1\ 0) = (0\ -1\ +1\ -1\ 0)$


Booth's multiplication(for understanding)



By **Bit Pair Booth Recoding of Multiplier** (this is main solution for problem)

( 0 -1 +1 -1 0)  $\rightarrow$  By bit pairing 0 [-1 +1] [-1 0]  $\rightarrow$  0 [-21 + 20] [-21 + 0]  $\rightarrow$  0 [-1] [-2]

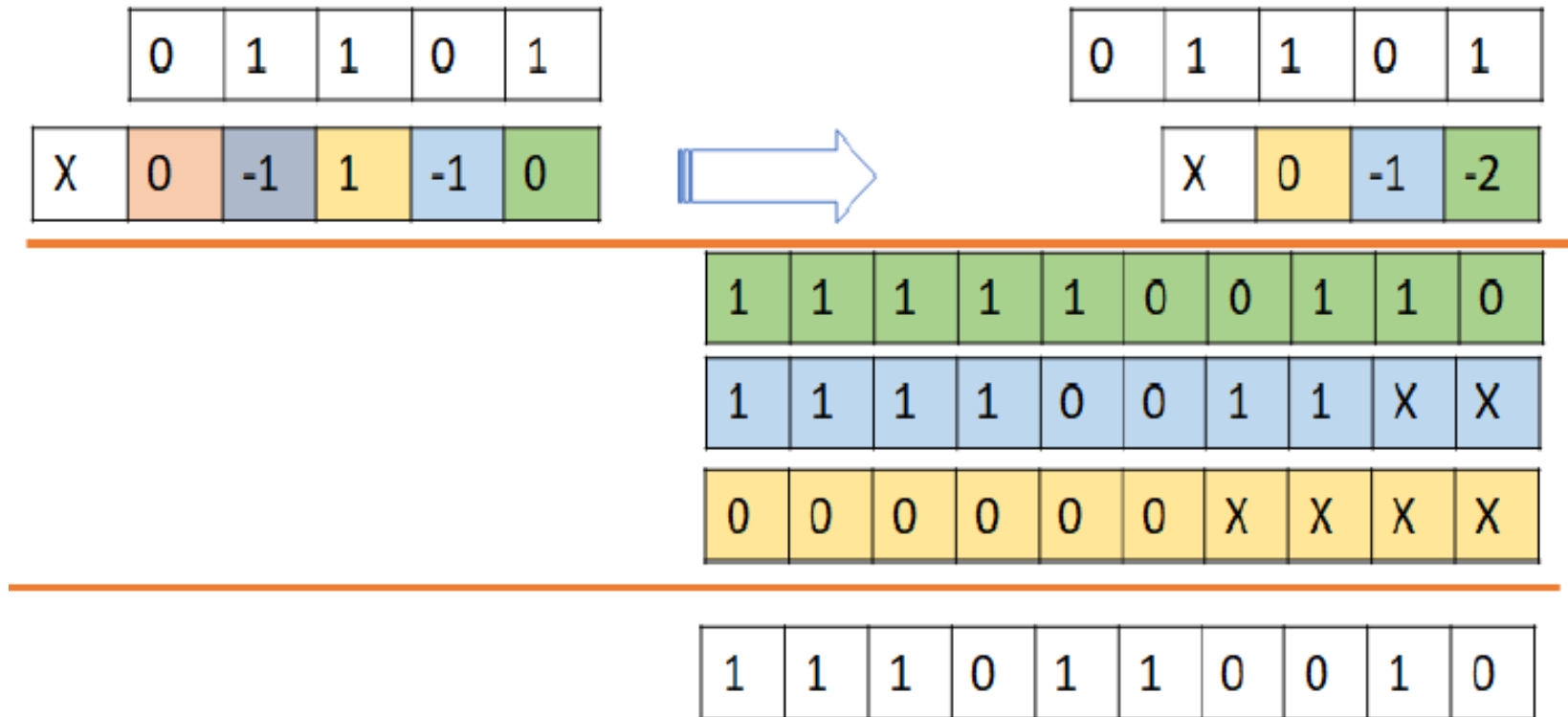- Now the Multiplicand is multiplied by Bit pair recoded multiplier ( 0, -1, -2)



### Example 2: The worst case of Booth Recoding Multiplier.

- In this example the given Multiplier is (0 1 0 1 0 1) and Multiplicand is (0 0 1 1 1 0).
- The recoding of Normal Multiplier using Booth Recoding and Bit pair is as shown below  
 $[0\ 1\ 0\ 1\ 0\ 1] \rightarrow [+1\ -1\ +1\ -1\ +1\ -1\ +1] \rightarrow [(+1,-1)\ (+1,-1)\ (+1,-1)] \rightarrow [+1\ +1\ +1]$
- It is clear the worst case of booth recoded Multiplier is also reduced to  $n/2$  summands in Bit pair Booth algorithm

**a) Normal Multiplier**

	0	0	1	1	1	0
x	0	1	0	1	0	1

**b) Booth Recoding Multiplier**

	0	0	1	1	1	0
x	+1	-1	+1	-1	+1	-1

**a) Bit Pair Recoded Multiplier**

	0	0	1	1	1	0
			x	+1	+1	+1

---

**Partial Products**

					0	0	1	1	1	0								
							0	0	1	1	1	0						
									0	0	1	1	1	0				
													0	0	1	1	1	0

---

**Final Product**

0	0	0	0	1	0	0	1	0	0	1	1	0
---	---	---	---	---	---	---	---	---	---	---	---	---



## Integer Division


examples of decimal division and binary division of the same values. Consider the decimal version first. The 2 in the quotient is determined by the following reasoning: First, we try to divide 13 into 2, and it does not work. Next, we try to divide 13 into 27.

We go through the trial exercise of multiplying 13 by 2 to get 26, and, observing that  $27 - 26 = 1$  is less than 13, we enter 2 as the quotient and perform the required subtraction. The next digit of the dividend, 4, is brought down, and we finish by deciding that 13 goes into 14 once, and the remainder is 1.

$$\begin{array}{r} 21 \\ 13 \overline{)274} \\ \underline{26} \phantom{0} \\ 14 \\ \underline{13} \\ 1 \end{array}$$

$$\begin{array}{r} 10101 \\ 1101 \overline{)100010010} \\ \underline{1101} \phantom{00000} \\ 10000 \\ \underline{1101} \phantom{0000} \\ 1110 \\ \underline{1101} \\ 1 \end{array}$$
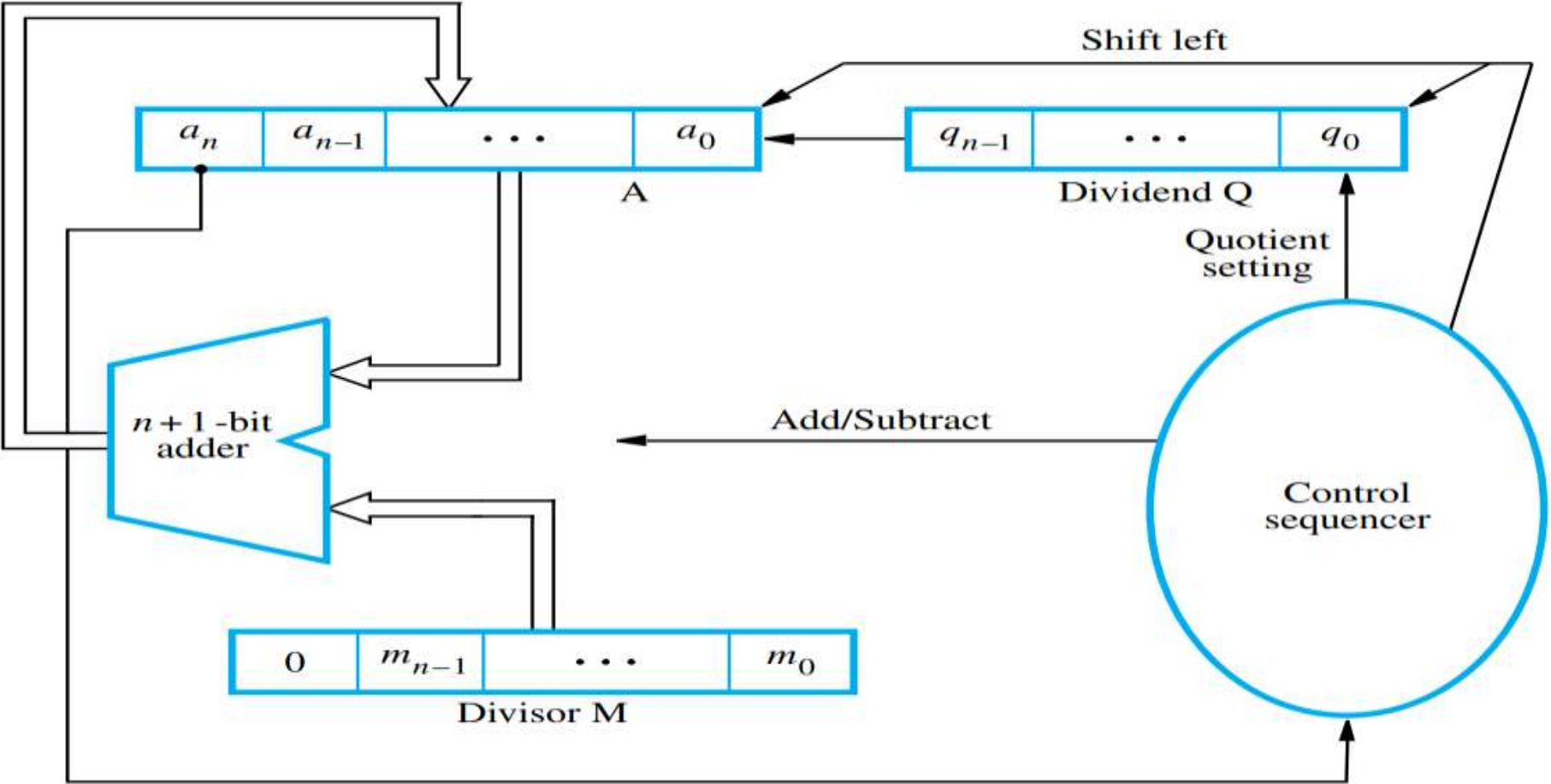
# Circuit arrangement for binary division



## Restoring Division

**Step 1:** In this step, the corresponding value will be initialized to the registers, i.e., register A will contain value 0, register M will contain Divisor, register Q will contain Dividend, and N is used to specify the number of bits in dividend.

**Step 2:** In this step, register A and register Q will be treated as a single unit, and the value of both the registers will be shifted left.


**Step 3:** After that, the value of register M will be subtracted from register A. The result of subtraction will be stored in register A.

**Step 4:** Now, check the most significant bit of register A. If this bit of register A is 0, then the least significant bit of register Q will be set with a value 1. If the most significant bit of A is 1, then the least significant bit of register Q will be set to with value 0, and restore the value of A that means it will restore the value of register A before subtraction with M.


**Step 5:** After that, the value of N will be decremented. Here n is used as a counter.

**Step 6:** Now, if the value of N is 0, we will break the loop. Otherwise, we have to again go to step 2.

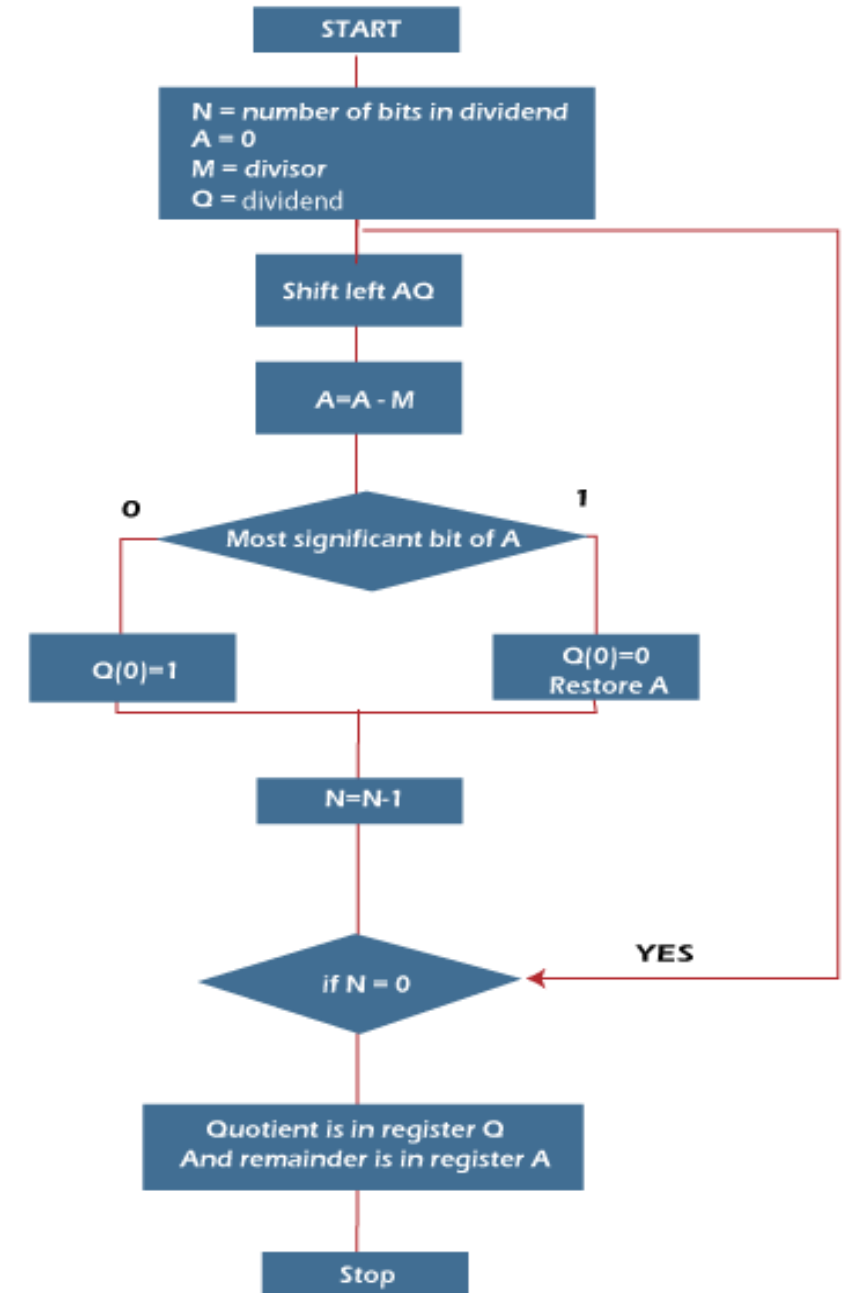**Step 7:** This is the last step. In this step, the quotient is contained in the register Q, and the remainder is contained in register A.




$$\begin{array}{r}
 10 \\
 11 \overline{) 1000} \\
 \underline{11} \\
 10
 \end{array}$$

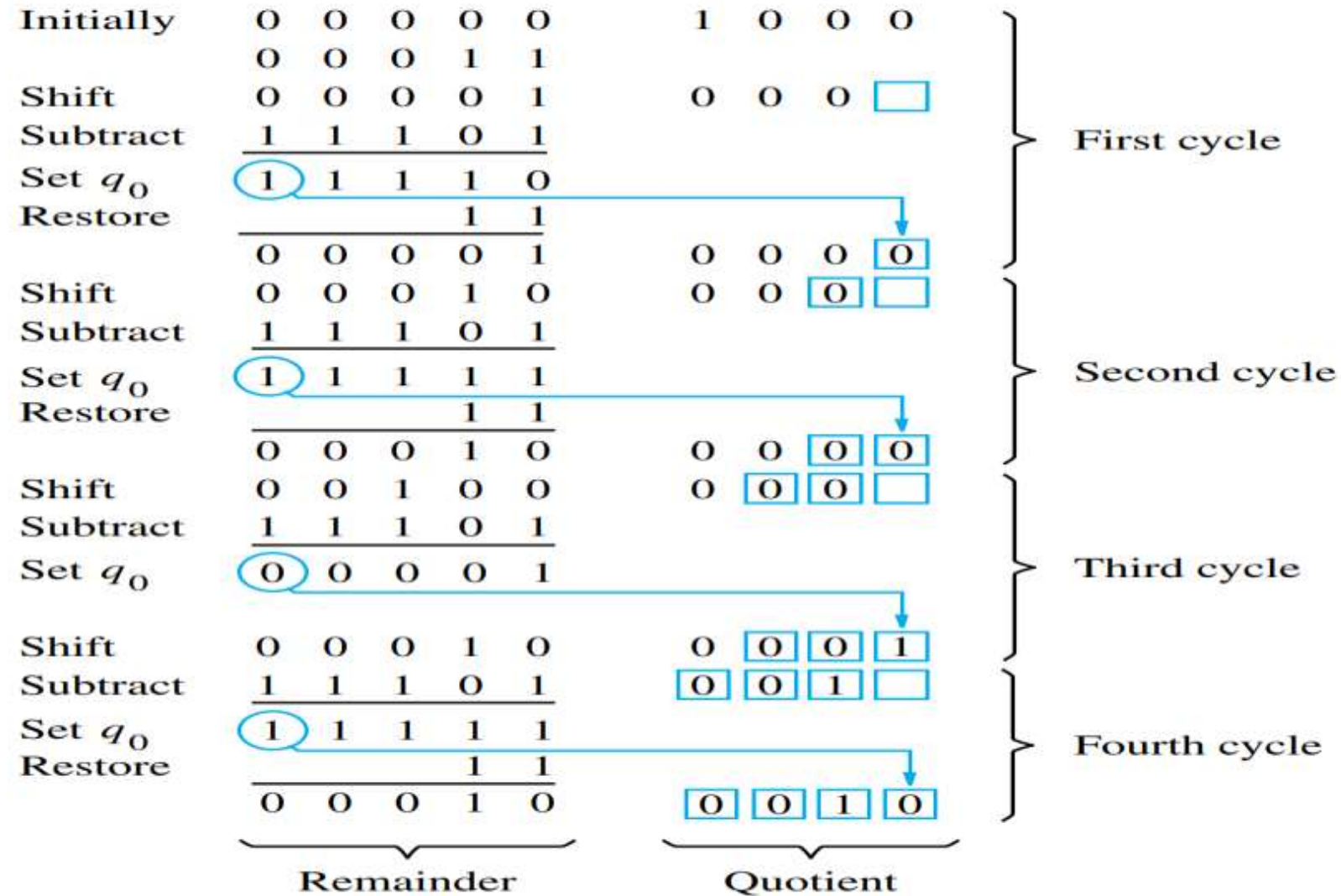

**Figure 9.24** A restoring division example.
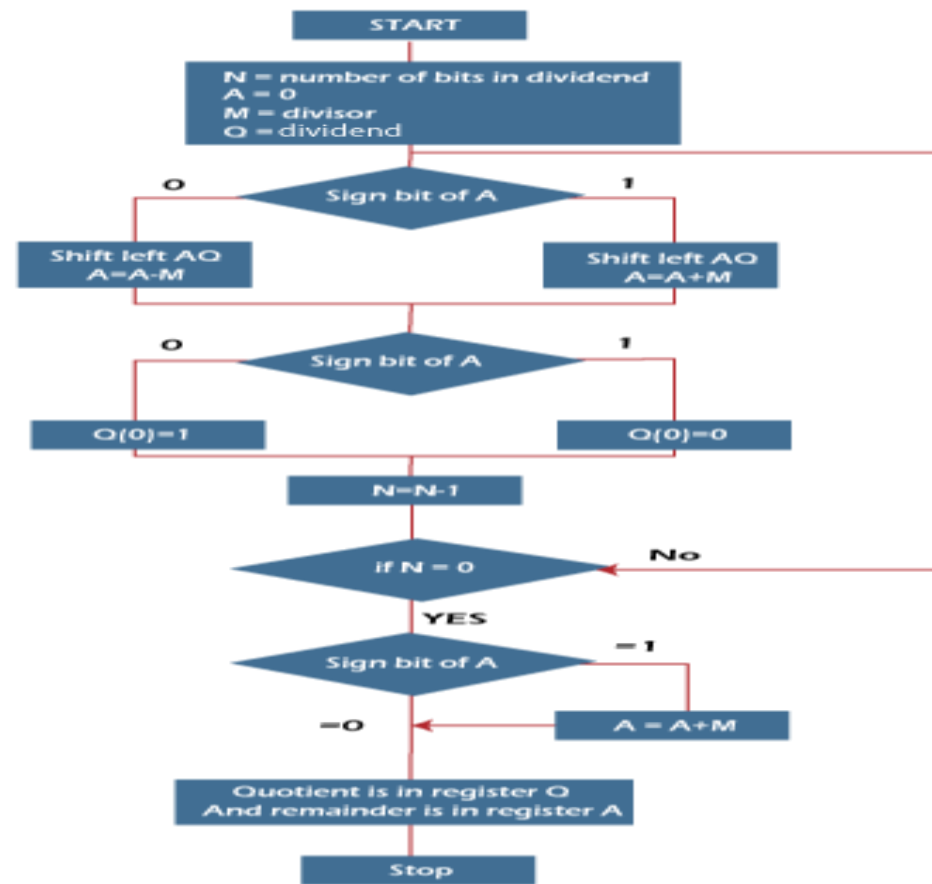
## non-restoring division algorithm

The non-restoring division algorithm is more complex as compared to the restoring division algorithm. But when we implement this algorithm in hardware, it has an advantage, i.e., it contains only one decision and addition/subtraction per quotient bit. After performing the subtraction operation, there will not be any restoring steps. Due to this, the numbers of operations basically cut down up to half. Because of the less operation, the execution of this algorithm will be fast.




- Step 1: (Repeat  $n$  times)

➤ If the sign of A is 0, shift A and Q left one bit position and subtract M from A; otherwise, shift A and Q left and add M to A.

➤ Now, if the sign of A is 0, set  $q_0$  to 1; otherwise, set  $q_0$  to 0.

 - Step2: If the sign of A is 1, add M to A



# Floating-Point Numbers and Operations

Go to unit 1 chapter 1 last topic

## Arithmetic Operations on Floating-Point Numbers

When adding or subtracting floating-point numbers, their mantissas must be shifted with respect to each other if their exponents differ.

Consider a decimal example in which we wish to add  $2.9400 \times 10^2$  to  $4.3100 \times 10^4$ . We rewrite  $2.9400 \times 10^2$  as  $0.0294 \times 10^4$  and then perform addition of the mantissas to get  $4.3394 \times 10^4$ .

The rule for addition and subtraction can be stated as follows:

### Add/Subtract Rule

1. Choose the number with the smaller exponent and shift its mantissa right a number of steps equal to the difference in exponents.
2. Set the exponent of the result equal to the larger exponent.
3. Perform addition/subtraction on the mantissas and determine the sign of the result.
4. Normalize the resulting value, if necessary.

Multiplication and division are somewhat easier than addition and subtraction, in that no alignment of mantissas is needed



## Multiply Rule

1. Add the exponents and subtract 127 to maintain the excess-127 representation.
2. Multiply the mantissas and determine the sign of the result.
3. Normalize the resulting value, if necessary.

## Divide Rule

1. Subtract the exponents and add 127 to maintain the excess-127 representation.
2. Divide the mantissas and determine the sign of the result.
3. Normalize the resulting value, if necessary.

## Implementing Floating-Point Operations


The hardware implementation of floating-point operations involves a considerable amount of logic circuitry. These operations can also be implemented by software routines.

In either case, the computer must be able to convert input and output from and to the user's decimal representation of numbers.

In many general-purpose processors, floating-point operations are available at the machine-instruction level, implemented in hardware



An example of the implementation of floating-point operations is shown in Figure

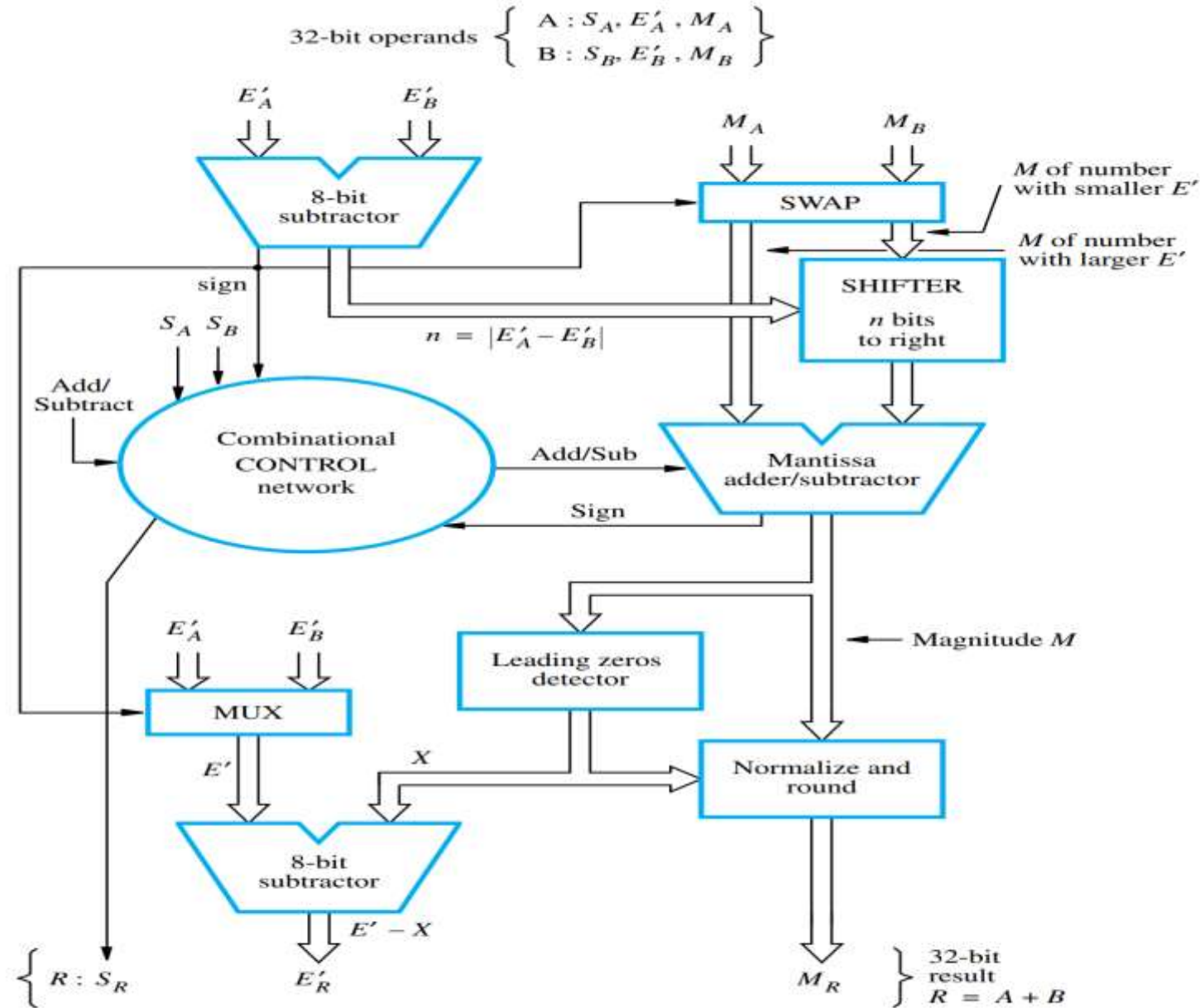

**Figure 9.28** Floating-point addition-subtraction unit.